

# Methods of output-voltage adjustment for DC/DC converters

By Chris Glaser

Member Group Technical Staff, Senior Applications Engineer

## Introduction

Some systems benefit by adjusting the output voltage of one or more DC/DC converters while the converters are enabled and the system is operating. Solid-state drives, smartphones and optical modules adjust the core voltage (usually through I<sup>2</sup>C communication) to the main processor to fine-tune performance and power consumption.

Other, simpler systems such as USB Type-C™ ports and lower-power microcontrollers (MCUs) use a single digital signal to adjust between two output voltages in order to adapt to power delivery demands or reduce power consumption in standby or sleep mode.

Modulators and drivers found in high-speed optical modules and optical line cards may require an adjustable supply voltage, such as a negative voltage for biasing optical circuits. Most LED drivers dim their light output through the same analog voltage or a filtered pulse-width modulation (PWM) signal technique. These types of output-voltage adjustment and their typical use cases are described with numerous applications across a variety of end equipments.


## Digital-communication interface

A digital-communication interface, like I<sup>2</sup>C, generally provides the most control when adjusting the output voltage. I<sup>2</sup>C requires a system with a communication interface, which in turn requires a host MCU to run the interface as the master device.

The output voltage can typically be set to a large number of discrete values within a given range and with a specific step size. For example, the TPS62866 allows output voltages between 0.4 V and 1.675 V in 5-mV increments. The host processor fine-tunes the output voltage to optimize power consumption and performance on the main processor's core rail. This is known as adaptive voltage scaling (AVS).

In some systems, the host processor is the same as the main processor. This processor controls its own core voltage, which changes based on the operating conditions and tasks being executed. The converter's default or startup voltage is critical because it must be high enough to properly boot the processor before the processor can

Figure 1. Example of using the VSET pin to set a converter's default or startup voltage

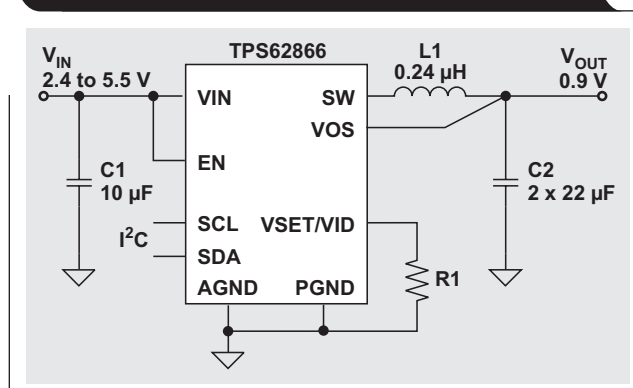

operate the I<sup>2</sup>C bus and program the output voltage.

Figure 1 shows an application schematic of the TPS62866 and its voltage-setting (VSET) pin, which enables setting the startup voltage in hardware before the I<sup>2</sup>C bus is active with resistor R1 based on the specific processor used.

The TPS62866 integrates a resistor-to-digital (R2D) converter on the VSET/VID pin, which reads this resistor value at startup and programs the device. Setting the output voltage with a VSET pin saves one feedback (FB) resistor (and its cost and size); increases output voltage accuracy by not including the inaccuracy of the two FB resistors; and provides lower leakage current because the resistor value is only measured at startup and consumes no current afterwards.

The main disadvantage of the VSET pin in devices without an I<sup>2</sup>C bus is that the output voltage cannot be changed during operation because the resistor value is only measured at startup. The TPS62866 overcomes this limitation by combining the VSET pin with a function for voltage identification definition (VID). After startup, the pin functions as a digital input to change the output

voltage. Table 1 shows the different configurations of output voltages and I<sup>2</sup>C addresses possible with the R1 resistor and VSET pin.


A digital-communication interface also allows much more system control, interaction and fault reporting. The TPS62866's I<sup>2</sup>C registers contain other settings, including device enable, device reset, programmable slew rate when changing output voltages, mode selection for either light-load efficiency or lowest ripple, overtemperature warning, current-limit indication, and power-good indication.

A power-management bus (PMBus), another digital-communication interface based on the I<sup>2</sup>C physical layer, allows digital control of a power supply with a communications protocol and command language. The main difference between PMBus and I<sup>2</sup>C is that no I<sup>2</sup>C code is required; with PMBus, the programming, monitoring and fault commands can be selected from a preselected command set. PMBus is usually used in applications with output voltage adjustment when high flexibility and reconfigurability are required. Figure 2 shows a typical PMBus multiphase application using the TPS40428 dual-phase, dual-output buck controller.

**Table 1. VSET pins set the startup output voltage with a single resistor within a predefined set of values**

R1 Resistor (E96 Series) at VSET/VID pin	Default Output Voltage (V)	Device Address
249 k	1.15 V	1000 110
205 k	1.10 V	1000 101
162 k	1.05 V	1000 100
133 k	1.00 V	1000 011
105 k	0.95 V	1000 010
86.6 k	0.90 V	1000 001
68.1 k	0.85 V	1001 000
56.2 k	0.80 V	1001 001
44.2 k	0.75 V	1001 010
36.5 k	0.70 V	1001 011
28.7 k	0.65 V	1001 100
23.7 k	0.60 V	1001 101
18.7 k	0.55 V	1001 110
15.4 k	0.50 V	1001 111
12.1 k	0.45 V	1000 000
10 k	0.40 V	1000 111

**Figure 2. TPS40428 dual buck controller with PMBus (PMBDATA, PMBCLK and SMBALERT pins)**

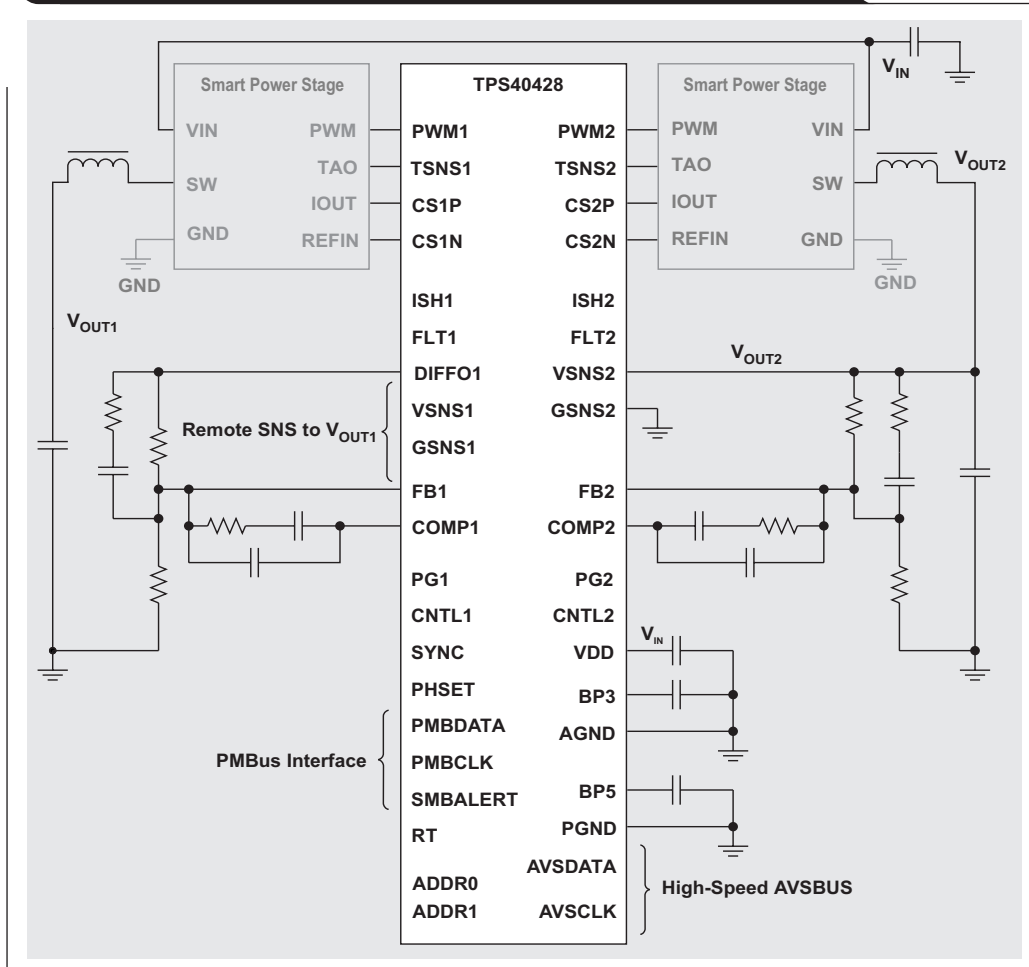

### Digital input(s)

A single digital-input signal is the simplest way to adjust the output between two voltages. This method requires a general-purpose input/output (GPIO) pin of the host MCU (or any other digital signal). Changing the output voltage between two states during operation is useful for USB Type-C ports, which deliver more power at voltages higher than 5 V. Some MCUs also use dynamic voltage scaling (DVS) to reduce power consumption in operating modes such as standby or sleep, which operate with a lower supply voltage. This is called a voltage select (VSEL) function and is a dedicated pin on some devices, such as the TPSM82480 and TPS62136.


The VSEL technique described in Reference 1 changes the voltage of a USB Type-C port from the standard 5-V to a higher 9-V fast-charging level. Figure 3 shows the typical VSEL circuit and Figure 4 shows the resulting change in output voltage. Generally, the output-voltage slew rate is not controllable when using a VSEL pin. The circuit's control loop operates quickly to bring the output voltage to the new regulation point.

Some VSEL pins operate with a VID function for powering processor-core voltage rails, where the connection of the VSELx pins directly controls the output-voltage set point. The margining transistor and resistor are internal. The VSELx pins can connect to fixed logic levels, MCU pins or discrete logic.


The TPS62866 shown in Figure 1 combines its VSET pin with a VID pin so that the startup voltage is set, then the output voltage is changed after startup through the same pin. The TPS62802 contains a similar multifunction pin with its VSEL/MODE pin. The VSEL portion operates like a VSET pin, setting the output voltage with a single resistor. After startup, the MODE function changes the device from power-save mode to a lower-noise and less-efficient forced PWM mode.

In some ultra-low-power devices, the FB resistors and connections are completely internal and the output voltage is only changed via the VSELx pins. This internal configuration can achieve much higher impedance to achieve ultra-low power and still be immune to noise coupling. With external FB resistors, the FB net is larger and therefore has greater coupling to other nets, which requires a higher FB resistor current. Table 2 shows 16 possible output voltage settings for the TPS62745 and its four VSELx pins. The VSELx pins are changeable during operation but do not allow output-voltage adjustment outside the listed values.

**Figure 3. A VSEL pin integrates the required transistor to achieve voltage margining through resistor R3**

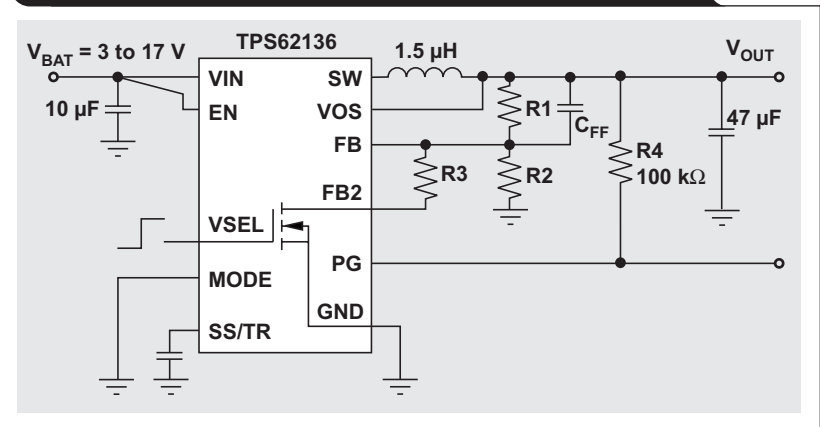

**Figure 4. Voltage margining through the VSEL pin changes the output voltage**

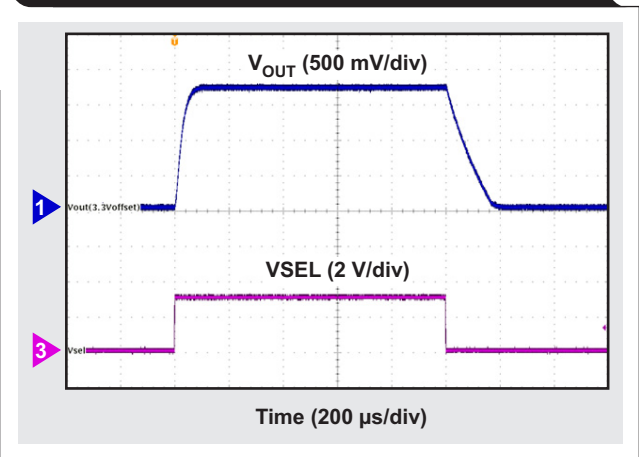

**Table 2. Some VSEL pins set the output voltage within a pre-defined set of values**

Device	V <sub>OUT</sub> (V)	VSEL 4	VSEL 3	VSEL 2	VSEL 1
TPS62745	1.8	0	0	0	0
	1.9	0	0	0	1
	2	0	0	1	0
	2.1	0	0	1	1
	2.2	0	1	0	0
	2.3	0	1	0	1
	2.4	0	1	1	0
	2.5	0	1	1	1
	2.6	1	0	0	0
	2.7	1	0	0	1
	2.8	1	0	1	0
	2.9	1	0	1	1
	3	1	1	0	0
	3.1	1	1	0	1
	3.2	1	1	1	0
	3.3	1	1	1	1

### Analog voltage input

The final type of output-voltage adjustment uses an analog signal to control the output voltage. This analog signal, fed into the FB pin through a resistor, is usually generated from a voltage reference, either a discrete voltage reference like the TLV431 or an analog output created from the voltage reference inside an MCU, the current or voltage output of a digital-to-analog converter (DAC), or a PWM signal filtered with a simple resistor-capacitor (RC) filter. With an analog voltage, any output voltage is attainable, instead of just discrete settings as with the previously discussed methods. This is critical for analog LED dimming, which requires a gradual change in light output instead of larger step changes. A fully adjustable output voltage also allows fine-tuning of analog-circuit behavior.

The filtered PWM-signal method requires just a single GPIO pin of an MCU, two resistors and one capacitor. Using a DAC instead of a PWM signal gives a cleaner output voltage, with no possibility of a PWM frequency appearing on the output rail. A DAC also eliminates issues arising from variation in the PWM signal's RC filter over temperature or component tolerance.

Reference 2 and Equations 1 through 3 show details of the necessary calculations for basic output-voltage adjustment from an analog voltage. Using the same calculations with the TPS62088 and DAC53608 generates an output voltage between 0.3 V and 1.8 V from a DAC output voltage between 0.3 V and 3 V. Figure 5 shows the tested schematic. Figure 6 shows measured data (with a 3.3-V input voltage and 1-A load) compared to the ideal curve, with nearly perfect matching. Equation 1 gives the transfer function of the analog voltage to the output voltage, while Equations 2 and 3 select the proper resistor values.

Figure 5. The DAC53608 adjusts the TPS62088's output voltage


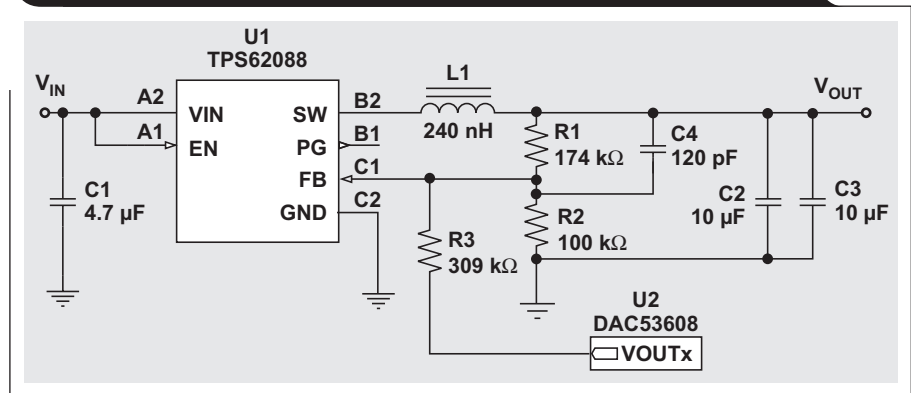


Figure 6. Comparison of measured output voltage adjustment to calculated

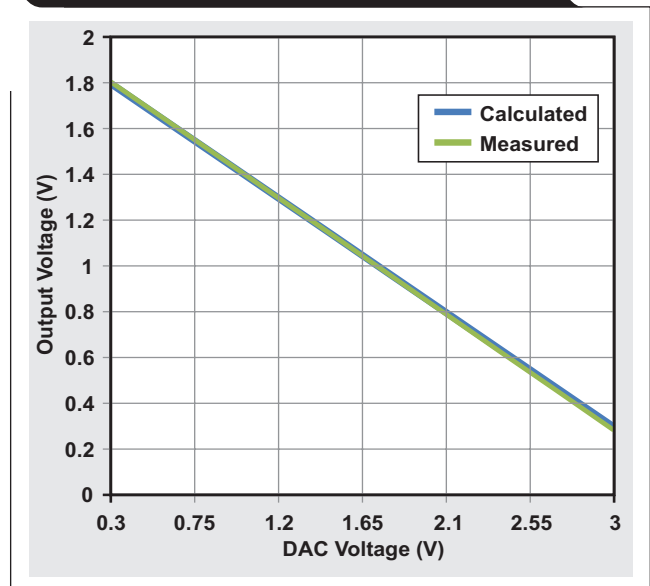

$$V_{OUT} = V_{FB} \left( 1 + \frac{R1}{R2} \right) - \frac{R1}{R3} (V_{DAC} - V_{FB}) \tag{1}$$

$$R2 = -V_{FB} \times R1 \times \frac{V_{DACLOW} - V_{DACHI}}{(V_{OUTLOW} - V_{OUTH} + V_{DACLOW} - V_{DACHI}) \times V_{FB} - (V_{DACLOW} \times V_{OUTLOW}) + (V_{DACHI} \times V_{OUTH})} \tag{2}$$

$$R3 = R2 \times R1 \times \frac{V_{DACHI} - V_{FB}}{(R2 \times V_{FB}) + (R1 \times V_{FB}) - (R2 \times V_{OUTLOW})} \tag{3}$$

A further benefit of the DAC53608 is that its disabled outputs have a defined ~10-kΩ pulldown, as Figure 7 shows. This internal pulldown resistor eliminates the disabled-to-enabled power-on glitch from the DAC's output, which can cause transients on the output voltage during startup. Such glitches can potentially have a catastrophic impact on the load.

Figure 8 uses this same analog voltage-margining technique for a negative voltage, based on Reference 3. Using the TPS82130 power module in the inverting buck-boost configuration creates a variable negative-output voltage, useful for optical circuit biasing. Figure 9 shows very good matching until the lowest output voltages.

Equation 4 gives the transfer function from DAC voltage to output voltage.

$$V_{OUT} = \frac{-\frac{V_{FB}}{R2} - \frac{V_{FB}}{R1} - \frac{V_{FB}}{R3} + \frac{V_{DAC}}{R3}}{\frac{1}{R1} + \frac{1}{R3}} \quad (4)$$

Figures 6 and 9 also show a hidden benefit of analog voltage margining: adding a voltage into the FB pin achieves output voltages below the converter's FB pin voltage. The margining circuit shown in Figure 5 achieves a 0.3-V output voltage even with the TPS62088's 0.6-V FB pin voltage, while Figure 8 achieves voltages below -0.5 V even with the TPS82130's 0.8-V FB pin voltage. Such circuits can also be used with a fixed analog voltage instead of an adjustable DAC. Reference 4 uses this method to increase LED driver efficiency.

If no available analog voltage exists, an RC filter can create one by filtering a PWM signal. The frequency is held constant, while the duty cycle varies to adjust the resulting analog voltage. Reference 5 explains such a circuit for LED dimming applications. For DC/DC converters, the PWM frequency should be above the control-loop bandwidth, to allow easier filtering and to prevent the control loop from gaining up the frequency of the PWM signal and appearing on the output voltage.

Figure 7. The DAC53608 has a ~10-kΩ resistance to ground at startup

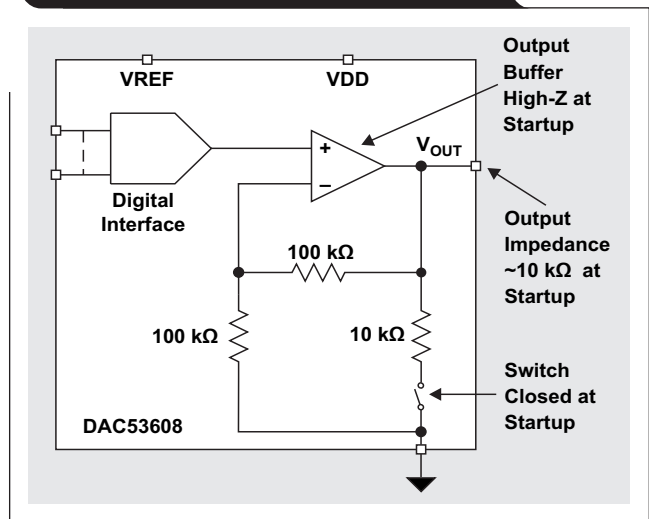


Figure 8. DAC53608 adjusts the TPS82130's negative output voltage


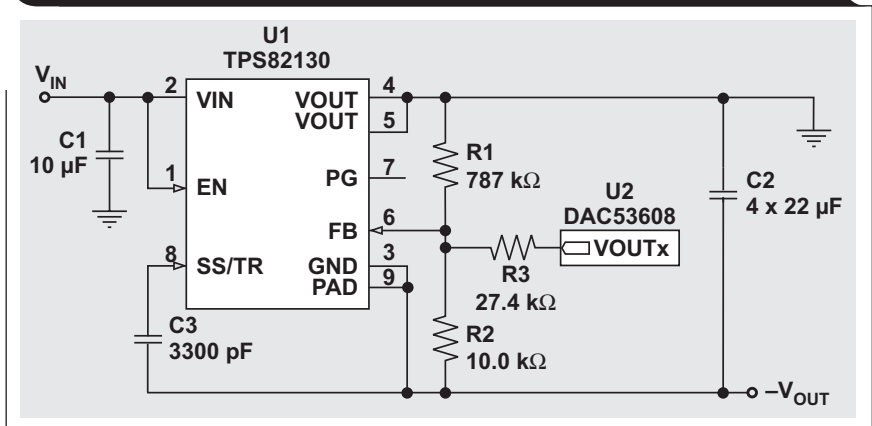


Figure 9. Comparison of measured negative output voltage adjustment to calculated

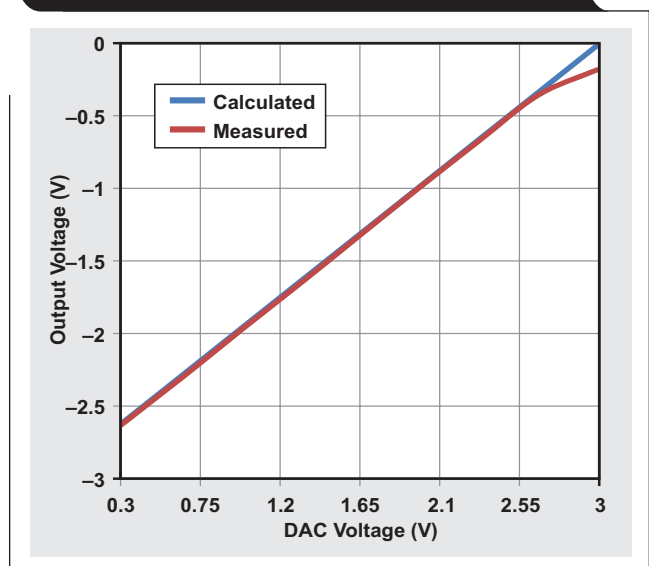

A 1-MHz PWM signal replaces the DAC shown in Figure 5 to create Figure 10, which shows that the RC-filtered PWM signal creates an analog voltage to adjust the TPS62088's output voltage. Figure 11 shows the margining performance. As the PWM signal's duty cycle increases, the analog voltage created by the RC filter increases and the output voltage decreases. To adapt Equation 1 to use with a PWM signal, replace  $V_{DAC}$  with  $[D \times V_{PWMHI} - (1 - D) \times V_{PWLLOW}]$  and  $R3$  with  $(R3 + R_{filter})$ .

Any of these three methods—DAC output, analog voltage or filtered PWM signal—generate an analog output that adjusts the output voltage. Simple systems use a filtered PWM signal or spare MCU analog output to adjust the voltage on one rail. As the number of voltages needing adjustment increases, a multichannel DAC becomes a more cost- and space-effective solution, since it's possible to control more DAC outputs on the same interface bus without an increase in MCU pins or additional circuitry. With the filtered PWM-signal method, every extra rail requires an additional MCU pin and RC filter.

Reference 6 is a calculator spreadsheet which aids in the design and analysis of both the positive- and negative-output voltage circuits shown in Figures 5 and 8.

### Conclusion

Changing the output voltage can optimize power delivery, reduce power consumption, or properly bias analog circuits such as LED drivers and optics. Three basic techniques—a digital communication interface, digital input and analog input—adjust the output voltage differently to match specific requirements. The examples shown in this article demonstrated common adjustment techniques that are transferable to your specific system and design challenges.

### References

1. "Voltage-Margining Power Supply for USB Type-C Ports in Docking Stations," Texas Instruments reference design (TIDA-01567).
2. Will Hadden, "Dynamically Adjustable Output Using TPS63000," Texas Instruments application report (SLVA251), August 2006.
3. "3- to 11.5-VIN, -5-VOUT, 1.5-A Inverting Power Module Reference Design for Small, Low-Noise Systems," Texas Instruments reference design (TIDA-01457).
4. Jeurgen Neuhaeusler, "Different Methods to Drive LEDs Using TPS630xx Buck-Boost Converters," Texas Instruments application report (SLVA419B), January 2012.

Figure 10. RC-filtered PWM signal controls the output voltage


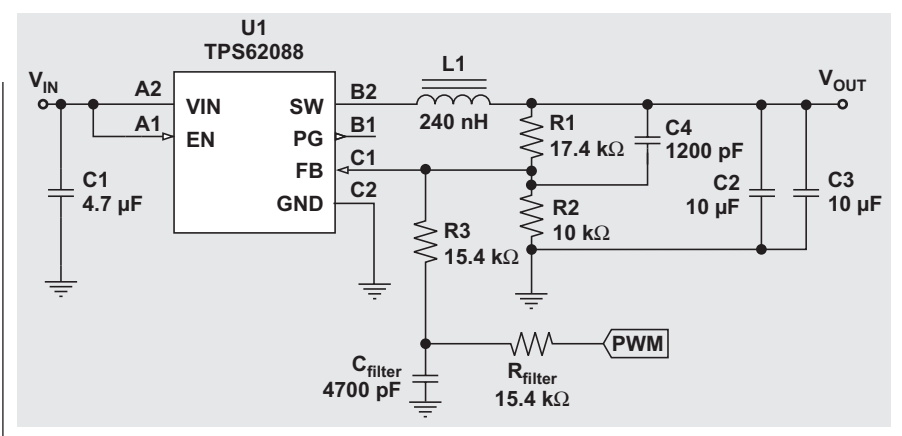


Figure 11. Output voltage margining by a PWM signal

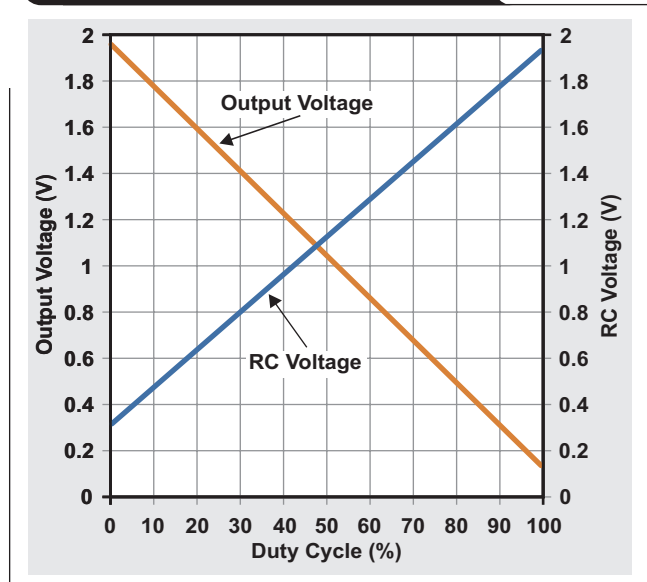

5. Matt Guibord, "How to Use Analog Dimming with the TPS6116x," Texas Instruments application report (SLVA471), July 2011.
6. Design Tool for Output Voltage Adjustment using a DAC (SLVC780), Texas Instruments, 2019

### Related Web sites

Product information:

**TPS62866, TPS40428, TPSM82480, TPS62136, TPS62802, TPS62745, TLV431, TPS62088, DAC53608, TPS82130**

## TI Worldwide Technical Support

---

### **TI Support**

Thank you for your business. Find the answer to your support need or get in touch with our support center at

[www.ti.com/support](http://www.ti.com/support)

China: <http://www.ti.com.cn/guidedsupport/cn/docs/supporthome.tsp>

Japan: <http://www.tij.co.jp/guidedsupport/jp/docs/supporthome.tsp>

### **Technical support forums**

Search through millions of technical questions and answers at TI's E2E™ Community (engineer-to-engineer) at

[e2e.ti.com](http://e2e.ti.com)

China: <http://www.deyisupport.com/>

Japan: <http://e2e.ti.com/group/jp/>

### **TI Training**

From technology fundamentals to advanced implementation, we offer on-demand and live training to help bring your next-generation designs to life. Get started now at

[training.ti.com](http://training.ti.com)

China: <http://www.ti.com.cn/general/cn/docs/gencontent.tsp?contentId=71968>

Japan: <https://training.ti.com/jp>

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A011617

E2E is a trademark of Texas Instruments. USB Type-C is a trademark of USB Implementers Forum. All other trademarks are the property of their respective owners.

© 2019 Texas Instruments Incorporated.  
All rights reserved.



SLYT777

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2019, Texas Instruments Incorporated