TI Designs: TIDA-01627 USB Type-C[™] PD Power Bank Reference Design

U TEXAS INSTRUMENTS

Description

This power bank reference design offers highlyintegrated USB Type-C[™] power delivery (PD) for charging notebooks. The key aspect of this design is to reduce the bill of materials (BOM) cost while maintaining the overall functionality. The design implements unique considerations for reducing quiescent current and covers all the required aspects to guide users through the part selection and trade-off considerations.

Resources

TIDA-01627	De
TPS65987D	Pro
BQ25703A	Pro
TPD8S300	Pro
TPS563200	Pro

Design Folder Product Folder Product Folder Product Folder Product Folder




Features

- Supports 5 V at 3 A, 9 V at 3 A, 14.8 V at 2 A, 15 V at 3 A, and 20 V at 2.25 A for Power Data Objects (PDOs)
- Supports up to 45 W of Power to Charge Portable Devices
- Automatically Charges After Connecting to USB PD Source

Applications

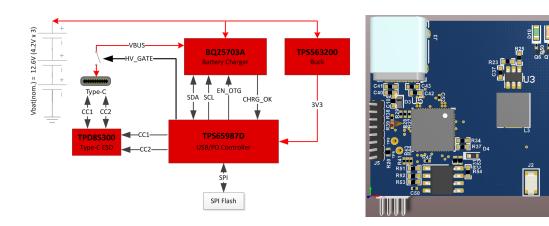- Charging Notebooks
- Charging Cell Phones
- Charging or Powering Other USB Type-C or PD Devices



53

An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.



1 System Description

For many, carrying multiple devices is a normal if not necessary part of daily life. The average user's dependency on these gadgets continues to increase while the overall battery life is decreasing. Many users have no choice but to carry an alternate portable source of power to help recharge gadgets while on the move. This reference design offers a power bank solution that can provide 45 W of power to charge a notebook while away from traditional power sources.

1.1 Key System Specifications

PARAMETER	SPECIFICATIONS
Number of batteries	Three cells
Type of batteries	Lithium-ion cells
Minimum output voltage	5 V
Maximum output voltage	20 V
Maximum power	45 W

Table 1. Key System Specifications



2 System Overview

This reference design has been built around two key components: TPS65987D and BQ25703A. TPS65987D is the PD controller which controls all of the USB Type-C[™] and PD negotiations, in addition to controlling the BQ25703A battery charger over I²C. This battery charger chip manages all the power and battery charging. The chip also works as a reverse buck-boost to provide power in on-the-go (OTG) mode. TPD8S300 provides protection from electrostatic discharge (ESD) and VBUS to CC short and the TPS563200 generates 3.3 V from the battery to power the PD controller.

2.1 Block Diagram

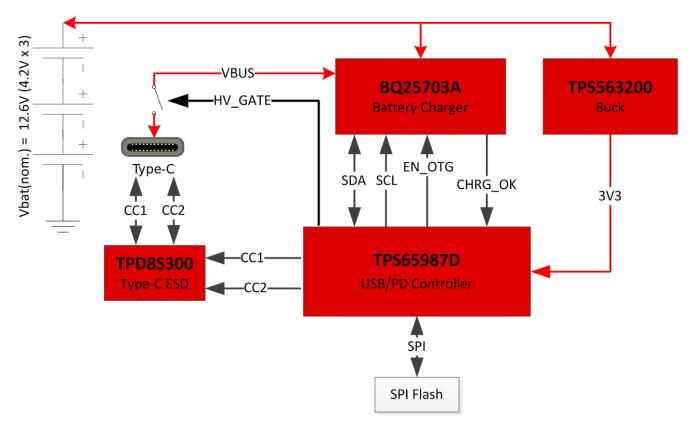


Figure 1. TIDA-01627 Block Diagram

2.2 Design Considerations

This TIDA-01627 system demonstrates how to manufacture reliable power banks using USB-Type-C and PD ports. To achieve this objective, the reference design uses the most-integrated USB-PD controller and battery controller in the market. The unique combination of these two devices ensures the most reliable and cost-effective solution to charge a notebook on the go.

This reference design has been tested with three lithium-ion cells; however, it can support one to four cells by simply changing the values of R12 and R14. For more details on this custom setting, see *bq25703A I2C Multi-Chemistry Battery Buck-Boost Charge Controller With System Power Monitor and Processor Hot Monitor*. Note that the batteries must be sized properly to support the PD load, which the power bank must also support.

The following subsections show the various parts of this design and the devices which they use.



2.2.1 TPS65987D USB Type-C[™] and PD Controller With Firmware Upgrade Capability

The TPS65987D is a highly-integrated USB Type-C and PD controller. This device is the brain of this system and is responsible for negotiating contract with the connected device, controlling various settings of the BQ25703A device. This device was chosen as it provides I²C master functionality, which can be configured to control any I²C slave by just using it's configuration utility.

Figure 2 shows the TPS65987D signals schematic. Figure 3 shows the TPS65987D power lines schematic.

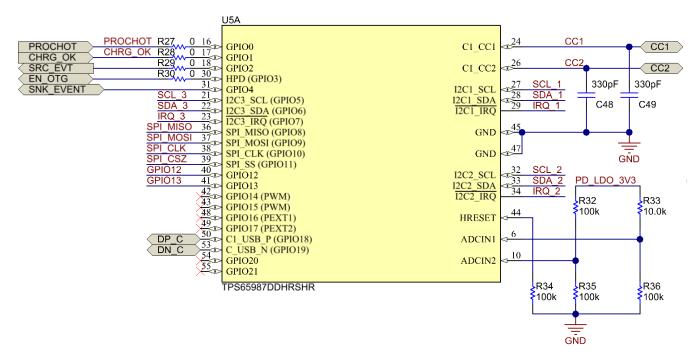


Figure 2. TPS65987D Signals Schematic



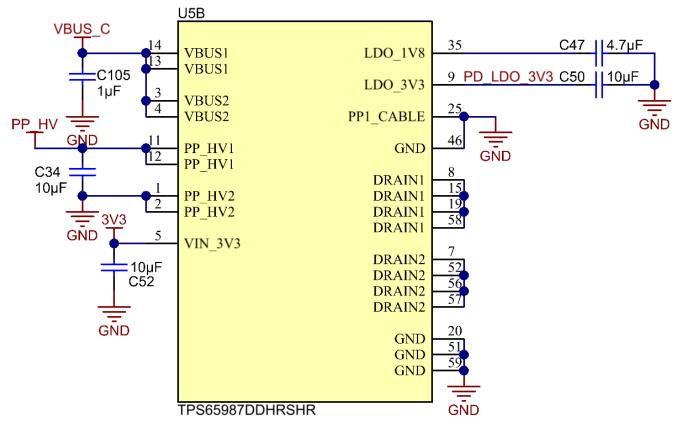


Figure 3. TPS65987D Power Lines Schematic



2.2.2 BQ25703A Multi-Chemistry, Battery Buck-Boost Charge Controller With System Power Monitor

The BQ25703A is a buck-boost, narrow-voltage DC (NVDC) charge controller for multi-chemistry portable applications such as notebooks and other mobile devices with rechargeable batteries. This device provides seamless transition between converter operation modes (buck, boost, or buck-boost), fast transient response, and high light-load efficiency. The BQ25703A takes input voltage from 3.5 V to 24 V and charges one to four batteries in series. The BQ25703A also supports USB On-The-Go (OTG) to provide a 4.48-V to 20.8-V output at the USB port.

This device is perfect for this reference design because it can work as a battery controller as well as a DC-DC converter. When the power bank is a sink and charging its own battery, then this chip assists with charging the batteries, whereas during the power source mode, this chip works as a DC-DC converter to generate the VBUS.

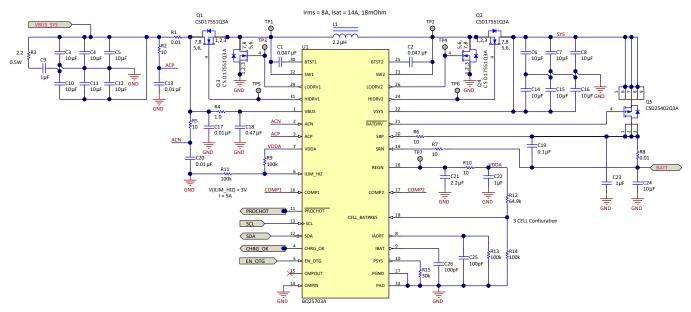


Figure 4. Battery Controller Schematic



2.2.3 TPD8S300 USB Type-C[™] Port Protector

The TPD8S300 is a single-chip, USB Type-C, port protection solution that provides 20-V short-to-VBUS overvoltage and IEC ESD protection. The TPD8S300 integrates four channels of 20-V short-to-VBUS overvoltage protection for the CC1, CC2, SBU1, and SBU2 pins of the USB Type-C connector. Additionally, IEC 61000-4-2 system level ESD protection is required to protect a USB Type-C port from ESD strikes generated by end-product users. The TPD8S300 integrates eight channels of IEC61000-4-2 ESD protection for the CC1, CC2, SBU1, SBU2, DP_T (top side D+), DM_T (top side D–), DP_B (bottom side D+), and DM_B (bottom side D–) pins of the USB Type-C connector. This integration means IEC ESD protection is provided for all of the low-speed pins on the USB Type-C connector in a single chip in the TPD8S300 device. Additionally, the CC and SBU lines require high-voltage IEC ESD protection that is 22-V DC tolerant to simultaneously support IEC ESD and short-to-VBUS protection. The TPD8S300 integrates this high-voltage IEC ESD diode and has been specifically designed to guarantee that it works in conjunction with the overvoltage protection field-effect transistors (FETs) inside the device. This sort of solution is very hard to generate with discrete components.

Figure 5 shows the TPD8S300 schematic.

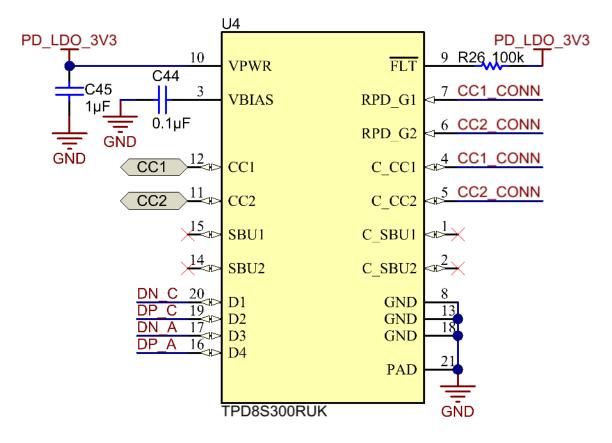


Figure 5. TPD8S300 Schematic

2.2.4 TPS563200 DC-DC Converter

The TPS563200 is an easy-to-use, synchronous step-down, DC-DC converter optimized for low standby current with minimum external components. A high switching frequency of typically 650 KHz allows the use of small inductors and provides fast transient response as well as high output voltage accuracy by using the D-CAP2[™] mode control. In this reference design, this DC-DC converter functions to generate the 3.3-V rail to power up the TPS65987D device. If nothing is connected to the power bank, then the enable input goes low and everything shuts down. If any PD power sink is connected to the power bank, then this input remains high for as long as the device is connected.



3 System Powering Scheme

This power bank reference design features two different power modes: power source mode and power sink mode.

3.1 Power Source Mode

In this mode, the power bank works as a source and the device connected to it draws power. To start in this mode, the user must press the S1 switch and then ensure that the device is connected after the LED turn on. The user can release this switch after connecting the device, after which it will no longer respond to further presses. If the device comes up as a sink, then the TPS65987D device drives the "SRC_EVT" node high, which ensures that U3 remains turned on even after S1 is released by maintaining 3.3 V at the SYS_EN node. The TPS65987D device drives the SRC_EVT node low when it detects disconnection, which forces the SYS_EN node down after some time, after which U3 eventually turns off and leads to a system shutdown.

Figure 6 shows a schematic of the 3.3-V power scheme of the power bank.

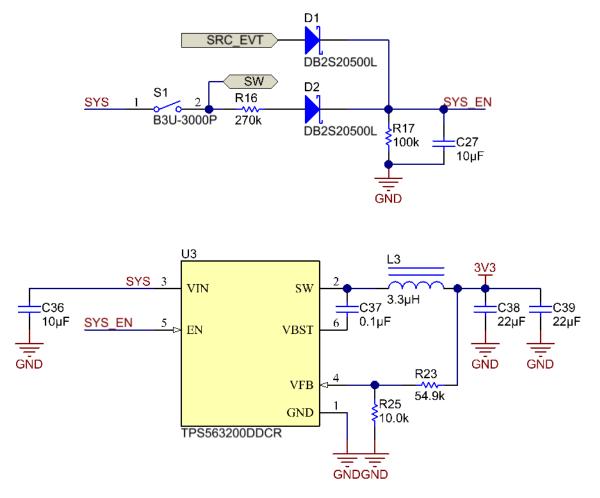


Figure 6. Schematic of 3.3-V Power Scheme of Power Bank

3.2 Power Sink Mode

8

Whenever the designer connects a PD source, this power bank begins charging in dead battery mode. The LED turn on automatically to indicate the charging status. Pressing the user switch S1 causes a power role swap and, if accepted by the connected device, causes the power bank to enter power source mode.



4 Test Data

The following subsections show the PD logs, which were taken during various use cases.

4.1 Power Bank When Charging Notebook

The power bank registers as a power source when the user presses the switch with the power bank connected to a notebook. The power bank sends its source power data object (PDO) and the notebook requests for the suitable PDO from the available options. From the given case in Figure 8, the power bank presents various PDOs, for which the notebook chooses a 20-V PDO.

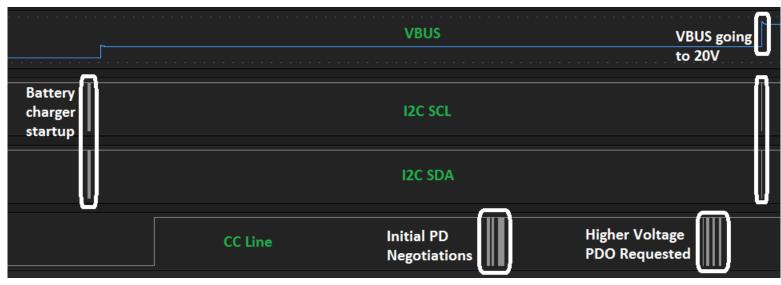


Figure 7. !~Varios signals during negotiations



Test Data

www.ti.com

OC Left) AttachWait.SRC ==> Attached.SRC @ 06 638 951 000					
Packet 0 CC Event CC1 Pins Ad Curr Left CC1 CC2 Time Time Time Stamp 3 Connected 3.0 A "PowerBank" Rp Open "Notebook" Rd Open 7.678 ms 6.638 951 000					
4 Packets Pont Sce ² CBL PD Msg Msg Type Cable Plug Msg ID Obj Cnt Extended Cmd Cmd Cmd Cmd Cmd Cold Clip Duration Time Time Time Stamp 4-7 "???" CBL Vendor Defined DFP or UFP 0 1 No Vom Header Discover Identity REQ 0 PD SID 633.528 us 7.221 ms 6.646 628 792					
4 Packets Left Sc PD Msg Msg Type DR PR Msg ID Obj Cnt Extended Fixed Max Cur Voltage Dual Role Fixed Max Cur Voltage Dual Role					
4 Packets Port Sort Msg Type Cable Plug Msg ID Obj Cht Extended Cmd Cmd Cmd Type Obj Pos Vendor Defined Duration Time Time Stamp 12-15 "???" CBL Vendor Defined DFP or UFP 0 1 No VDM Header Discover Identity REQ 0 PD SID 633.717 us 7.220 ms 6.840 571 016					
Packet Left SRC PD Msg Msg Type DR PR Msg ID Obj Cnt Extended Fixed Max Cur Voltage Dual Role Fixed Max Cur Voltage Dual Role					
Packet Right SCP Msg Type DR PR Msg ID Obj Cnt Duration Idle Time Stamp 1 17 "Notebook" SNK 0 0 493.637 us 7.196 ms 6.849 062 736					
Packet Right SSP SSP Msg Type DR PR Msg ID Obj Cnt Request Max Opr Cur Opr Cur Cap Mismatch Obj Pos Duration Idle Time Stamp 18 "Notebook" Figure UFP SNK 0 1 1.50A 1.50A 0 5 625.779 us 74.557 us 6 .856 752 736					
Packet Left SRC Msg Type DR PR Msg ID Obj Cnt Duration Idle Time Stamp 19 "PowerBank" SRC O 0 499.597 us 1.043 ms 6 . 857 453 072					
Packet Left SRC Msg Type DR PR Msg ID Obj Cnt Duration Idle Time Stamp 20 "PowerBank" SRC DFP SRC 1 0 499:597 us 116.483 us 6 . 858 996 016					
Packet Right SCP SNK PD Msg Msg Type DR PR Msg ID Obj Cnt Duration Idle Time Stamp 1 21 "Notebook" SNK GoodCRC UFP SNK 1 0 493.935 us 39.042 ms 6 .859 612 096					
Packet Left SRC SRC Msg Type DR PR Msg ID Obj Cnt Duration Idle Time Stamp 22 "PowerBank" SRC PS Ready DFP SRC 2 0 499.448 us 115.712 us 6 .899 148 096					

Figure 8. PD Log When Using Power Bank as Source



4.2 Power Swap Upon Switch Press

If the user connects the power bank to a notebook without pressing the switch, then the power bank registers as a sink and starts drawing power from the laptop. In this condition, the user can press the switch and perform a power role reversal to start charging the notebook. The following logs in Figure 9 show the power role sequence after pressing the switch.

CC Left) Attached.SNK @ 00.000 000 000 CC Right) Attached.SRC @ 00.000 000 000	
CC Event	CC2 Time Time Stamp Open 2.841 sec 0 . 000 000 000
D Packet ' Left Sore SNK 'PD Msg Msg Type DR PR Msg ID Obj Cnt Duration Idle 1 "PowerBank" ← SNK 'PD Msg PR Swap UFP SNK 4 0 499.597 us 105.819 us 3	Time Stamp 2 . 841 359 136
Packet Right SRC PD Msg Msg Type DR PR Msg ID Obj Cnt Duration Ide 2 "Notebook" SRC PD Msg GoodCRC DFP SRC 4 0 493.637 us 142.427 us	Time Stamp 2 . 841 964 552
Packet Right SRC Msg Type DR PR Msg ID Obj Cnt. Duration Idle 3 "Notebook" SRC Accept DFP SRC 6 0 493.637 us 75.299 us	Time Stamp 2.842 600 616
Packet Left SOP SNK PD Msg Msg Type DR PR Msg ID Obj Cnt Duration Time 4 "PowerBank" SNK PD Msg GoodCRC UFP SNK 6 0 499.597 us 2.229 ms	Time Stamp 2.843 169 552
0 Packet CC Event CC1 Pins Ad Curr PowerBank" ~ "Notebook" ~	CC2 Idle Time Stamp ~ 9.681 ms 2.845 399 000
0 Packet CC Event CC1 Pins Ad Curr Left CC1 CC2 Right CC1 (6 CC Event "PowerBank" Rd Open "Notebook" ~	CC2 Idle Time Stamp ~ 23.830 ms 2.855 080 000
	CC2 Time Time Stamp Open 169.620 ms 2.878 910 000
Packet Right SPC SP DR Mag Type DR PR Msg ID Obj Cnt Duration Idle	Time Stamp 3 . 048 530 168
Packet Left SOP SNK PD Msg Msg Type DR PR Msg ID Obj Cnt Duration Idle 9 "PowerBank" SNK PD Msg GoodCRC UFP SNK 7 0 492.744 us 1.784 ms	Time Stamp 3 . 049 083 544
0 Packet / Left SRC SOP PD Msg Msg Type DR PR Msg ID Obj Cnt Duration Idle	Time Stamp 3 . 051 360 668
Packet Right SRC PD Msg Msg Type DR PR Msg ID Obj Cnt Duration Time 11 "Notebook" SRC PD Msg GoodCRC DFP SRC 5 0 473.759 us 2.147 ms	Time Stamp 3 . 051 972 376
CC) Left) Attached.SNK ==> Unattached.SNK ==> Unattached.SRC @ 03.054 119 000 CC Right) Attached.SRC ==> Unattached.SN	NK @ 03.054 119 000))
	CC2 Ide Time Stamp Open 1.600 ms 3 . 054 119 000
CC Left) Unattached SRC ==> AttachWait SRC @ 03.055 719 000)CC Right) Unattached SNK ==> AttachWait SNK @ 03.055 719 00	
CC Event	CC2 Time Time Stamp Open 50.480 ms 3 . 055 719 000
Packet Left SRC 14 "PowerBank" SRC PD Msg Msg Type DR PR Msg ID Obj Cnt Fixed Source Cap UFP SRC 0 5 Fixed 3.00 A 5.00 V 0 Fixed 3.00 A 5.00 V 0	Max Cur Voltage Dual Role Fixed Max Cur Voltage Dual Role Cur Duar Fixed Max Cur Voltage Dual Role Cur Duar Fixed Max Cur Voltage Dual Role Cur Duar Fixed Max Cur Voltage Dual Role Fixed Duar Fixed Max Cur Voltage Dual Role Cur Duar Fixed Max Cur Voltage Dual Role Fixed Duar Fixed Max Cur Voltage Duar Fixed F
Packet Right SoP SNK PD Msg Type DR PR Msg ID Obj Cnt Duration Idle 15 "Notebook" ← SNK PD Msg GoodCRC DFP SNK 0 0 493.637 us 651.179 us	Time Stamp 3 . 107 481 496
Packet 'Right Sor SNK 'PD Msg Type DR PR Msg ID Obj Cht Request Max Opr Cur Opr Cur Cap Mismat 16 "Notebook" ← SNK 0 1	Itch Obj Pos Duration Idle Time Stamp 5 626.346 us 72.414 us 3 . 108 626 312
Packet Left SRC → Msg Type DR PR Msg ID Obj Cnt Duration Idle 17 "PowerBank" SRC → GoodCRC UFP SRC 0 0 499.448 us 1.043 ms	Time Stamp 3.109325072
Packet Left SRC → Msg Type DR PR Msg ID Obj Cnt Duration Idle 18 "PowerBank" Accept UFP SRC 1 0 499.448 us 115.776 us	Time Stamp 3 . 110 867 912
Packet Right SOF SNK PD Msg Msg Type DR PR Msg ID Obj Cnt Duration Idle 19 "Notebook" ← SNK GoodCRC DFP SNK 1 0 493.786 us 38.941 ms	Time Stamp 3.111 483 136
Packet Left SRC ⇒ Msg Type DR PR Msg ID Obj Cnt Duration Idle 20 "PowerBank" PS PS Ready UFP SRC 2 0 499.001 us 113.063 us	Time Stamp 3 . 150 918 312
Packet Right SCP SNK PD Msg Type DR PR Msg ID Obj Cnt Duration Time Stamp 21 "Notebook" ← SNK GoodCRC DFP SNK 2 0 493.786 us 3 . 151 530 376	

Figure 9. PD Log During Power Role Swap



Test Data

4.3 Power Bank Charging From PD Power Adapter

The power bank registers as a PD sink and makes a PD contract when it is connected to a PD power adapter. The power bank picks up the right PDO from the available options and starts charging (see Figure 10).

) CC) Left) Disabled @ 00 000 000 000) CC) Right) Unattached SRC@ 00 000 000 000 000 000 000 000 000 00
Packet OCEvent CC1 Pins Ad Our Left CC1 CC2 Idle Time Stamp 0 0 -
) CC Left) Disabled ==> Unattached SNK @ 03.430 248 000)
Openation CC1 Pins Ad Our Left CC1 CC2 Idle Time Stamp 0 1 Open "PowerBank" Rd Open "Charger" Rp Open 1.600 ms 3 .430 248 000
CC) Left) Unattached SNK ==>AttachWait SNK @ 03 431 848 000)CC) Right) Unattached SRC ==>AttachWait SRC @ 03 431 848 000)
U Packet OC Event CC1 Pins Ad Curr Left CC1 CC2 Right CC2 Idle Time Stamp 0 2 Connected 3.0A "PowerBank" Rd Open "Charger" Rp Open 126,637 ms 3.431 848 000
000 Left) AttachWait SNX ==> Attached SNX @ 03.558 485 000)00 Right) AttachWait SRC @ 03.558 485 000)
U Packet OCE Vent Col Pins Ad Curr * Left CC1 CC2 Time Time Stamp 0 3 Connected 3.0 A **PowerBank* Rd Open *Charger* Rp Open 108.094 ms 3.558 485 000
4 Packets Right SRC Msg Type DB PM sg ID Obj Cht Extended Max Cur Voltage Dual Role Fixed Max
Packet Left \$\$\$\$\$ The set of th
Packet Left \$\$\$\$\$ Note: \$\$\$ Note: \$\$ Note: \$\$\$ Note: \$\$ Note: \$\$ Note: \$\$\$ Note
Packet Right SRC Mag Type DR PR Mag ID Obj Cnt Duration Idle Time Stamp 1 10 *Charger* SRC O 0 503.769 us 1.405 ms 4.119 619 912
Packet Right SRC Msg Type DR PR Msg U Obj Cnt Extended Duration Idle Time Stamp 1 *Charger FD Msg U Obj Cnt Extended Duration Idle Time Stamp 503.769 us 73.611 us 4.121 529 032 Discourt Stamp Stamp
Packet Left \$50 WerBank NMsg Type DR PR Msg ID Obj Cnt Duration Idle Time Stamp 12 "PowerBank" GoodCRC UFP SNK 1 0 498.852 us 180.811 ms 4.122 108 312
Packet Right SRC Mag Type DR PR Mag ID Obj Crit Extended Duration Idle Time Stamp 13 *Charger* PS Ready DFP SRC 2 0 No 503.173 us 73.623 us 4.283.218 616
Packet Left \$\$\$ 14 \$\$\$ NK PD Msg Msg Type DR PR Msg ID Obj Cnt Duration Time Stamp 1 14 "PowerBank" \$\$\$ SNK UFP SNK 2 0 498.852 us 4.283793312

Figure 10. PD Log During Power Bank Charging



5 Design Files

5.1 Schematics

To download the schematics, see the design files at TIDA-01627.

5.2 Bill of Materials

To download the bill of materials (BOM), see the design files at TIDA-01627.

5.3 Layout Prints

To download the layer plots, see the design files at TIDA-01627.

5.4 Gerber Files

To download the Ferber files, see the design files at TIDA-01627.

5.5 Assembly Drawing

To download the assembly drawings, see the design files at TIDA-01627.

6 Related Documentation

1. Texas Instruments, bq25703A I2C Multi-Chemistry Battery Buck-Boost Charge Controller With System Power Monitor and Processor Hot Monitor Data Sheet

6.1 Trademarks

E2E, USB Type-C, D-CAP2 are trademarks of Texas Instruments. USB Type-C is a trademark of USB Implementers Forum, Inc. All other trademarks are the property of their respective owners.

7 Terminology

- BOM— Bill of materials
- ESD— Electrostatic discharge
- FET— Field-effect transistor
- LED— Light-emitting diode
- NVDC— Narrow voltage DC
- OTG— On-the-go
- PD— Power delivery
- **PDO** Power data object



Revision History

www.ti.com

Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from Original (April 2018) to A Revision		Page
•	Changed TPS65983B to TPS65987D throughout document	. 1
•	Changed TPD6S300 to TPD8S300 throughout document	. 1
•	Changed TPS62170 to TPS563200 throughout document	. 1
•	Changed block diagram and board images	. 1
•	Changed information in Section 2.2.1	. 4
•	Changed Figure 2	. 4
•	Changed Figure 3	. 5
•	Changed Figure 5	. 7
•	Changed information in Section 2.2.4	. 7

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ('TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your noncompliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products http://www.ti.com/sc/docs/stdterms.htm), evaluation modules, and samples (http://www.ti.com/sc/docs/stdterms.htm), evaluation

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2018, Texas Instruments Incorporated