

Test Data For PMP7919 2/20/2013






Vin	5.5V – 16V (change input/output caps and FETs if need to handle load dump)
Vout	11.84V
lout Max	15A
Fsw	450kHz per phase

FABRICATION


Board Dimensions: 4" x 3"

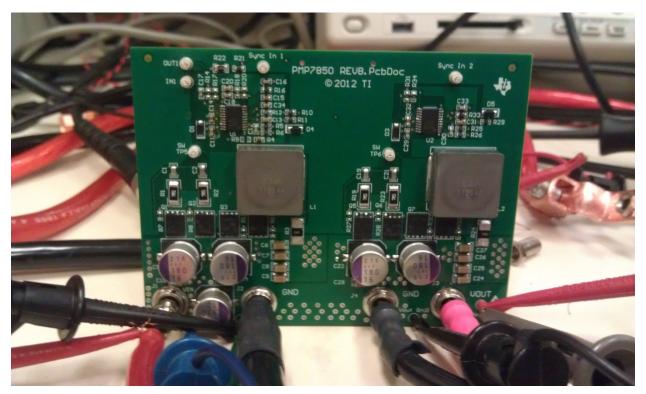

Top Side



SCHEMATIC

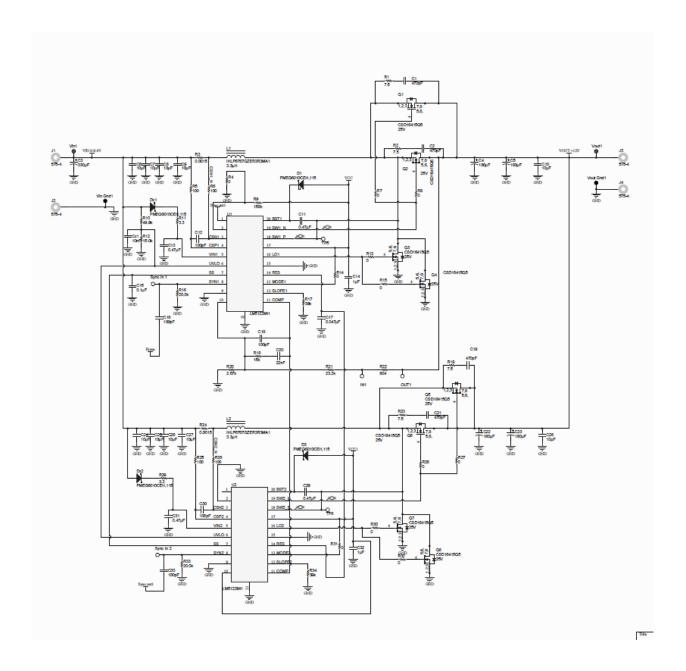


Note: Q1 to Q8 are BSC050NE2LS



Thermal Image #1...

Vin = 9.5V lout = 15A FETs... CSD16415's 25V $Rds_on= 1.5m\Omega \ (Vgs=4.5V)$ $Qg = 21nC \ (Vgs=4.5V)$

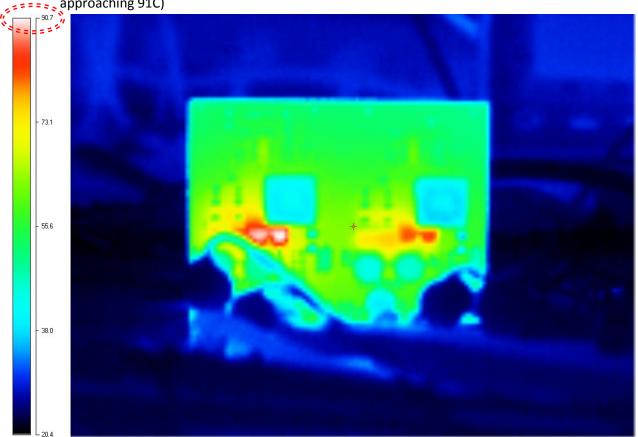
Comments...Board was on for 3 minutes at Vin 9.5 volts at max load 15A. (Notice Q3 and Q4 approaching 91C)





Thermal Image #2...

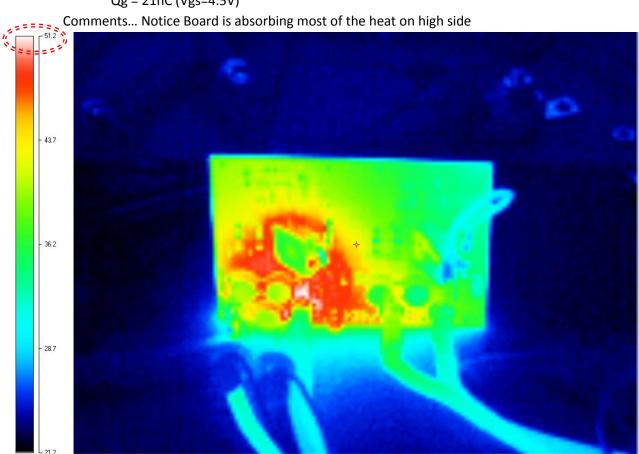Vin = 13V lout = 15A FETs... CSD16415's 25V Rds_on= $1.5m\Omega$ (Vgs=4.5V) Qg = 21nC (Vgs=4.5V)





Thermal Image #3...

Vin = 10V lout = 15A


FETs...BSC050NE2LS's

25V

Rds_on= $3m\Omega$

Qg = 10.4nC



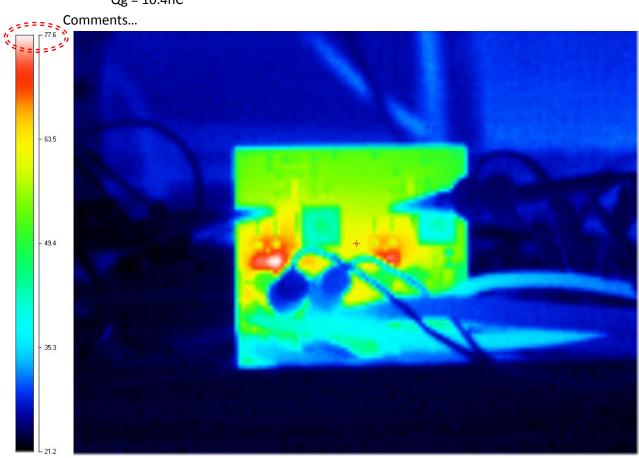




Thermal Image #4...

```
Vin = 10.5V
lout = 15A
FETs...
V
Rds\_on = m\Omega
Qg = nC
Comments...
```

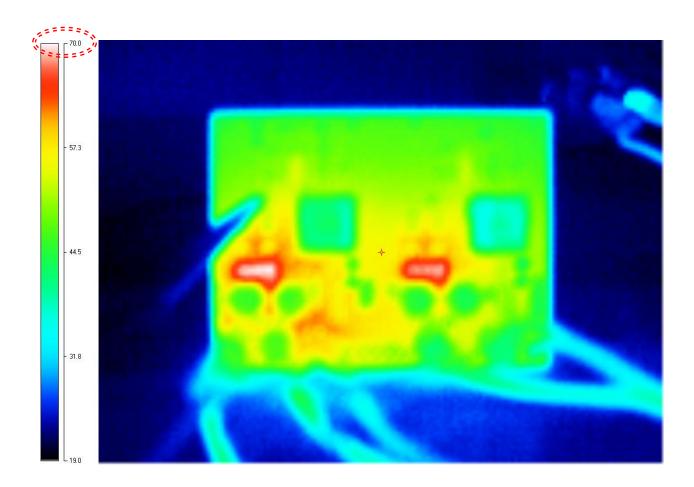Vin 10.5 Volts load is at 15A with the 40V FET's (CSD16413Q5A) All 8 of them. Max Temp is 72C.






Thermal Image #5...


```
\label{eq:Vin} \begin{split} \text{Vin} &= 10 \text{V} \\ \text{Iout} &= 15 \text{A} \\ \text{FETs...} \\ & \text{V} \\ & \text{Rds\_on= } m\Omega \\ & \text{Qg = nC} \\ \text{Comments...} \end{split}
```

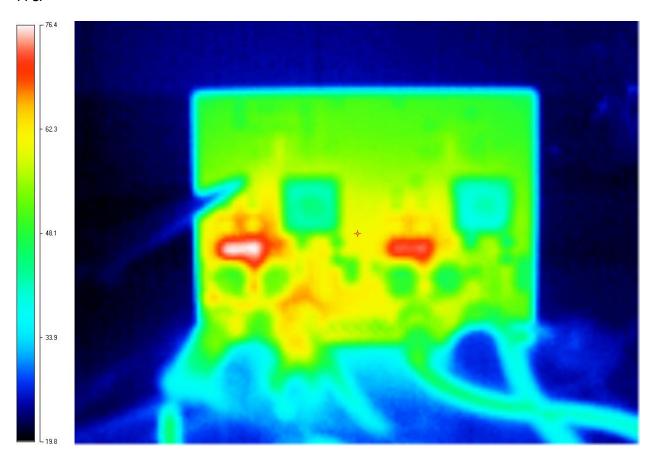Vin 10.5 Volts load is at 15A with the 40V FET's (CSD16413Q5A) Q4 and Q8 are removed. Max Temp is 77C.





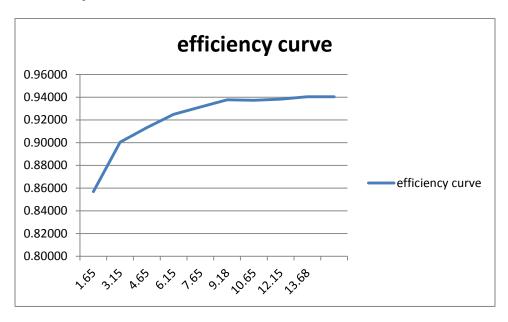Efficiency Curve with original FETs CSD16415



Efficiency Curve Data

Vin	lin	Vout	lout	Pin	Pout	Ploss	EFF
9.5	2.4	11.84	1.65	22.8	19.536	3.264	0.85684
9.5	4.36	11.84	3.15	41.42	37.296	4.124	0.90043
9.5	6.35	11.847	4.65	60.325	55.08855	5.23645	0.91320
9.5	8.292	11.846	6.15	78.774	72.8529	5.9211	0.92483
9.5	10.24	11.844	7.65	97.28	90.6066	6.6734	0.93140
9.5	12.204	11.843	9.18	115.938	108.7187	7.21926	0.93773
9.5	14.165	11.842	10.65	134.5675	126.1173	8.4502	0.93720
9.5	16.14	11.841	12.15	153.33	143.8682	9.46185	0.93829
9.5	18.13	11.84	13.68	172.235	161.9712	10.2638	0.94041
9.5	20.118	11.839	15.18	191.121	179.716	11.40498	0.94033



Current Sharing #1

Vin = 9.5Vin


lout = 15A

Channel 1 =

Channel 2 =

Channel 3 =

Comments... CH1 Current average is 10.2A

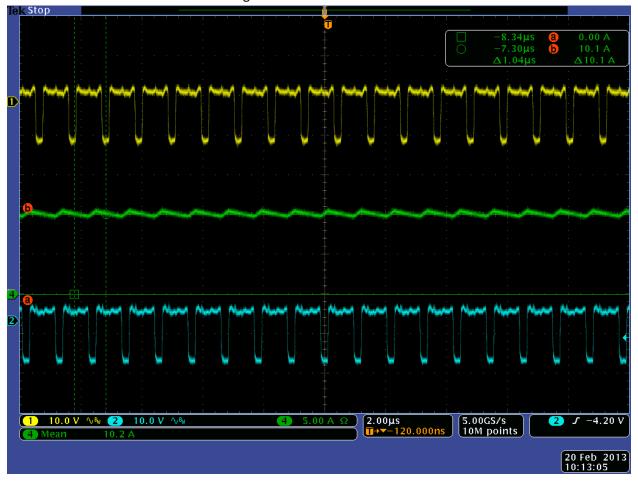



Current Sharing #2

Vin = 9.5V


lout = 15A

Channel 1 =

Channel 2 =

Channel 3 =

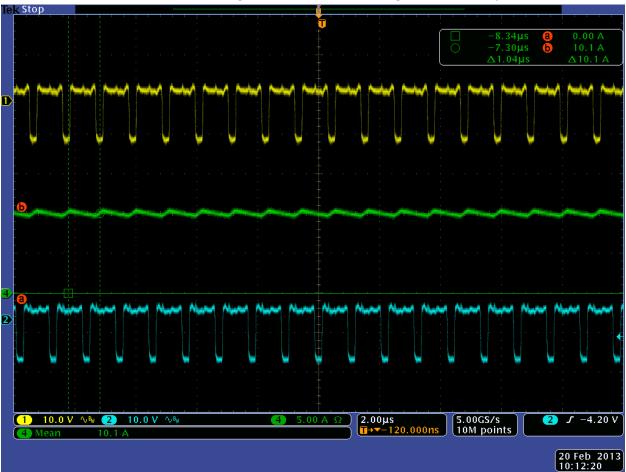Comments... CH2 Current average is 10.1A, Current Sharing between the 2 phases is +/- .5%






Input Line Transient #1

Vin = 13.2V down to 5.5V (2.7ms) then up to 9V (700ms)

Iout = 15A

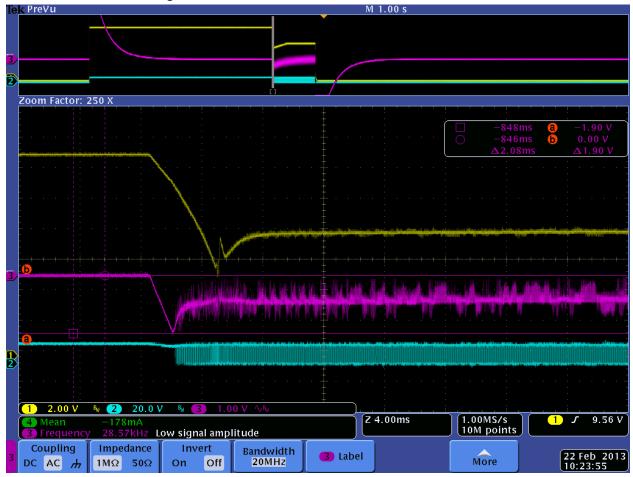Comments...No extra output capacitor, Deviation from Vout (right side of perturbation) 1.1V. Recommend setting vout to 11.6V and above to clear the 10.5V Vout min level






Input Line Transient #2

Vin = 13.2V down to 5.5V (2.7ms) then up to 9V (700ms)

Iout = 7.5A

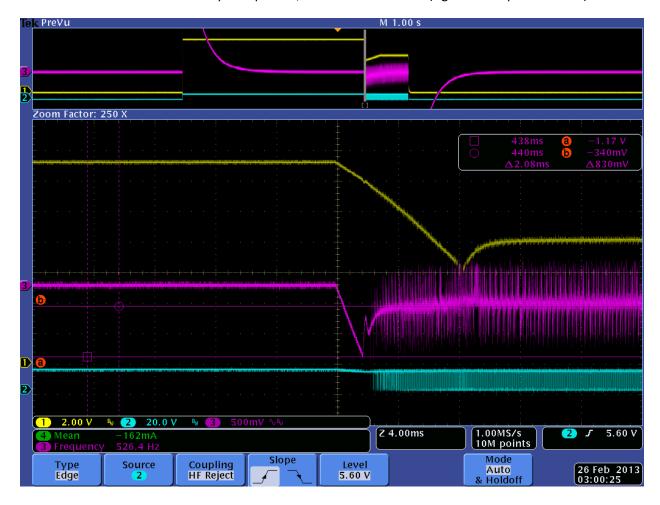Comments...No extra output capacitor, Deviation from Vout (right side of perturbation) 1.17V.




Input Line Transient #3



Vin = 13.2V down to 5.5V (2.7ms) then up to 9V (700ms)

lout = 3.5A

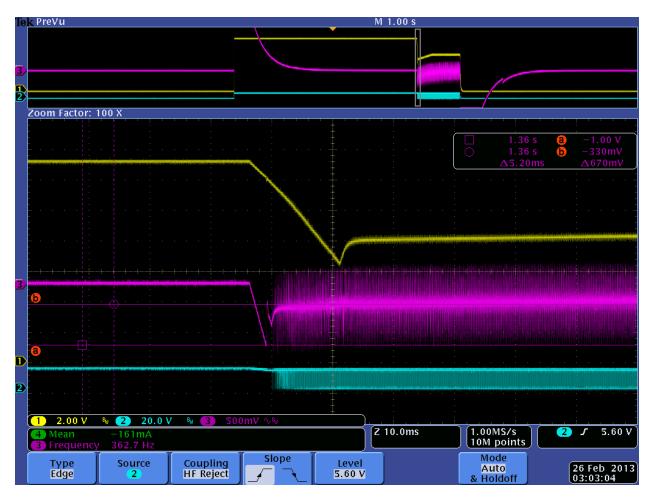Comments...No extra output capacitor, Deviation from Vout (right side of perturbation) 670mV.




Input Line Transient #4

Vin = 13.2V down to 5.5V (2.7ms) then up to 9V (700ms)



lout = 3.5A

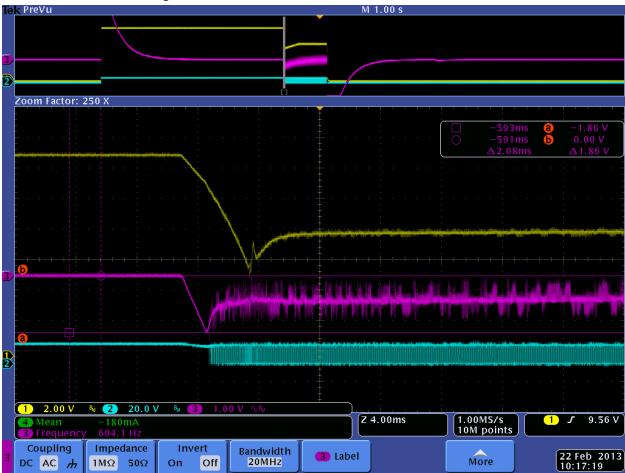Comments...1,000 μ F added to output cap, Deviation from Vout (right side of perturbation) 1.0V. Recommend setting Vout to 11.5V and above to clear the 10.5V Vout min level




Input Line Transient #5

Vin = 13.2V down to 5.5V (2.7ms) then up to 9V (700ms) lout = 3.5A



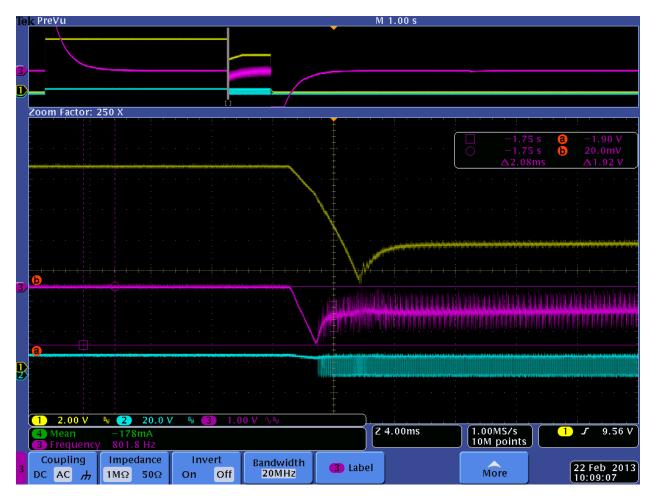Comments...2,000 μ F added to output cap, Deviation from Vout (right side of perturbation) 1.0V. Recommend setting Vout to 11.5V and above to clear the 10.5V Vout min level



Output Voltage Ripple #1

Vin = 9.5V

lout = 15A


Channel 1 =



Channel 3 =

Channel 4 =

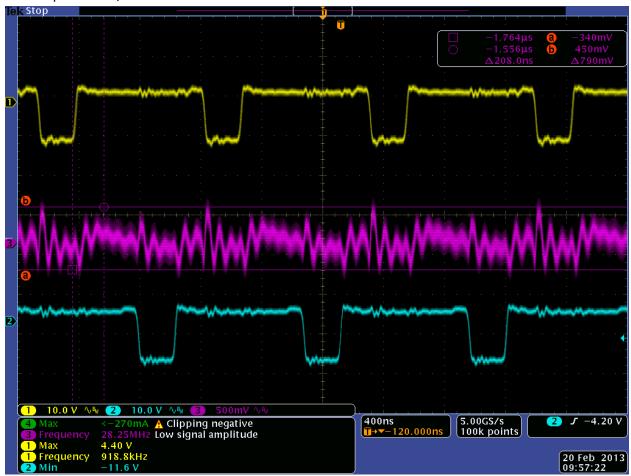Comments... 790mVpk-pk ripple, CH2 Current average is 10.1A, Current Sharing between the 2 phases is +/- .5%



Load Transient #1

Vin = 9.5V

lout = 7.5A to 15A ($100mA/\mu s$, 1kHz, 50% duty cycle)

Channel 3 = Output voltage







Startup Waveforms #1

Vin = 9.5V


Iout = No Load

Channel 1 = Switch node of phase 1 ()



Channel 3 = Vout

Comments...

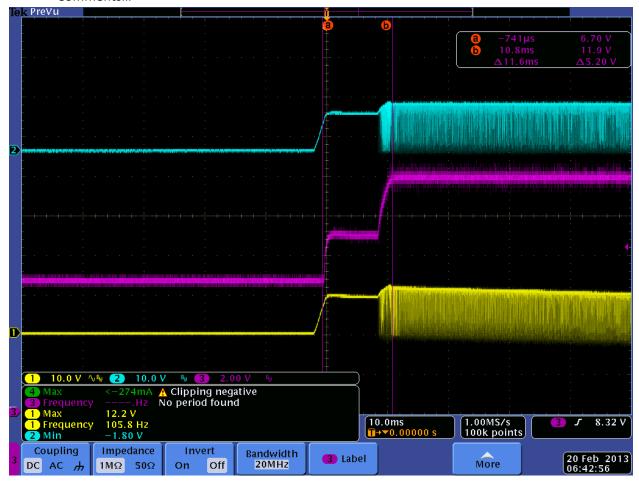

Startup Waveforms #2

Vin = 9.5V

Iout = 15A (Full load)


Channel 1 = Switch node of phase 1 ()

Channel 2 = Switch node of phase 2 ()



Channel 3 = Vout

Comments...

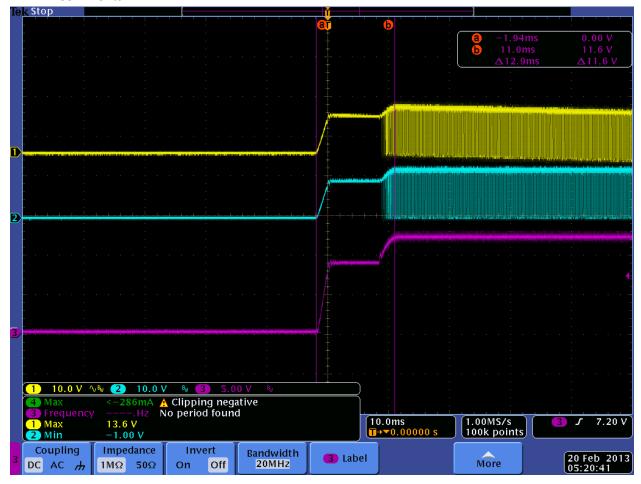

Startup Waveforms #3

Vin = 13V

Iout = No Load


Channel 1 = Vin

Channel 2 = Switch node of phase 2 ()



Channel 4 = Vout

Comments...

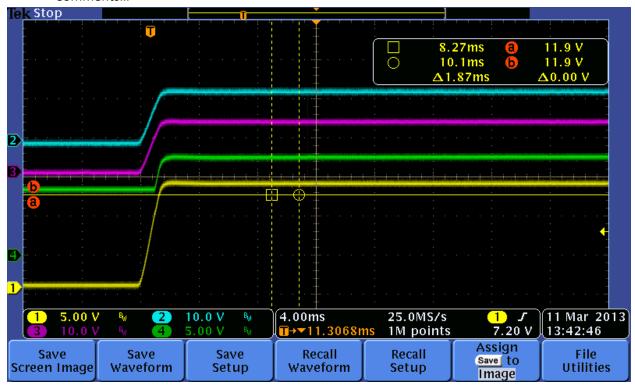

Startup Waveforms #4

Vin = 13V

lout = 15A


Channel 1 = Vin

Channel 2 = Switch node of phase 2 ()



Channel 4 = Vout

Comments...

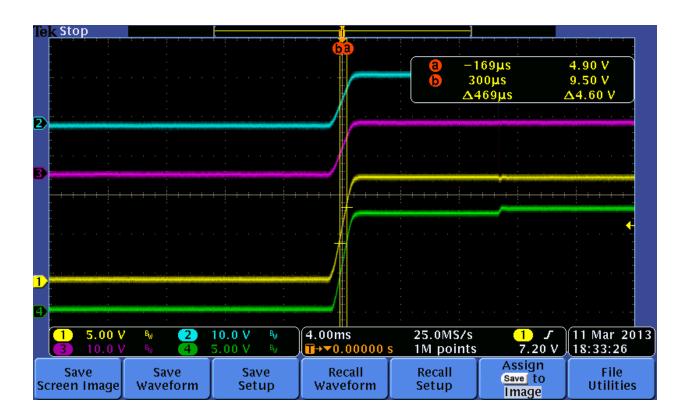

Startup Waveforms #5

Vin = 12V

Iout = No Load


Channel 1 = Vin

Channel 2 = Switch node of phase 2 ()



Channel 4 = Vout

Comments...

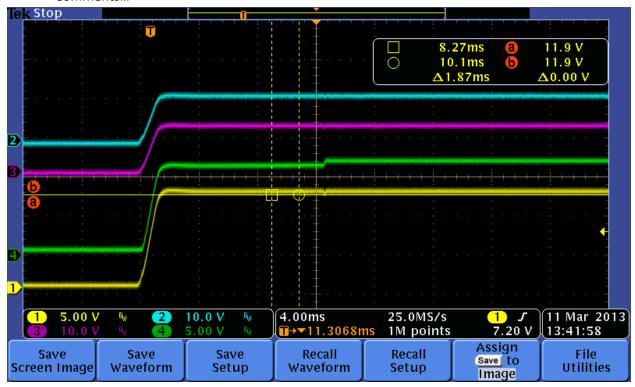

Startup Waveforms #6

Vin = 12V

lout = 15A


Channel 1 = Vin

Channel 2 = Switch node of phase 2 ()



Channel 4 = Vout

Comments...

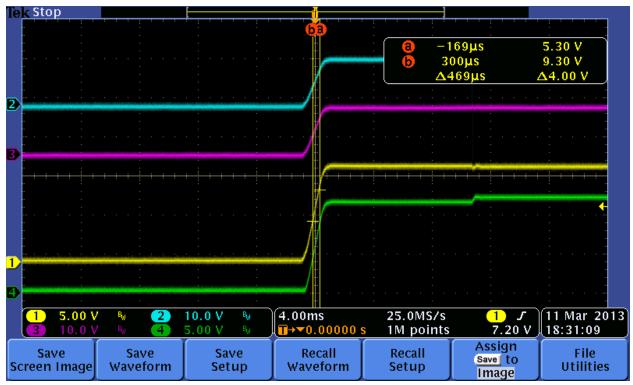

Startup Waveforms #7

Vin = 11V

lout = No Load


Channel 1 = Vin

Channel 2 = Switch node of phase 2 ()



Channel 4 = Vout

Comments...

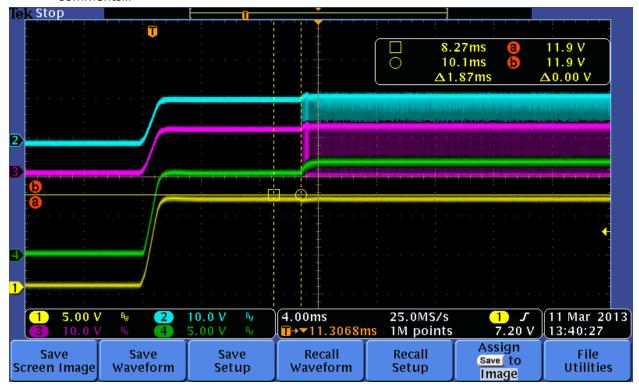

Startup Waveforms #8

Vin = 11V

lout = 15A


Channel 1 = Vin

Channel 2 = Switch node of phase 2 ()



Channel 4 = Vout

Comments...

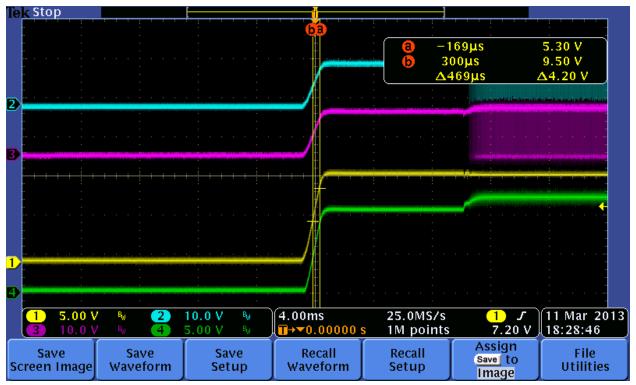

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design. TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have *not* been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.