

# Test Report of 2W Wide Input Buck Bias Supply <u>PMP7668</u>







# <u>CONTENTS</u>

# Contents

I.	INTRODUCTION
II.	DESCRIPTION
III.	BLOCK DIAGRAM
IV.	SPECIFICATIONS
V.	TEST SETUP
VI.	BOARD ASSEMBLY DRAWINGS4
VII.	LAYOUT5
VIII	EFFICIENCY AND REGULATION
a.	Performance Data
b.	Plots
IX.	WAVEFORMS
a.	Switching Node Waveforms
b.	Output Ripple9
c.	Turn On Characteristics
d.	Transient response
Х.	CONDUCTED EMISSIONS
XI.	SCHEMATIC
XII.	BILL OF MATERIALS14
XIII	CONCLUSION
XIV	APPENDIX



#### L INTRODUCTION

The following document is a compilation of test results of the PMP7668 reference design, a 2W bias supply using UCC28722 in buck configuration. The test results are taken over an input voltage range of 80V – 275V AC and 400V – 705V DC, driving a load up to 200mA.

#### П. DESCRIPTION

The PMP7668 is developed with the UCC28722 controller IC. The design is targeted for small form factor (69mm x 26mm) bias power solutions, especially for applications like e-metering. The differentiating feature of this design is its ability to operate over a wide input range (110 – 500VAC). It can work down to 80VAC with reduced output current. The design has an operating efficiency of around 70% at full load, with a voltage regulation of +/- 1%. Regulation, efficiency, output ripple, startup and switching stress of the design were tested under various conditions and are documented in this report. The circuit has an optional 3.3V output also.

#### **BLOCK DIAGRAM** III.



#### IV. **SPECIFICATIONS**

Input Voltage Range: 110VAC - 500VAC Output Voltage: 10V +/- 1V Output Current: 200mA Board Form Factor: 69mm x 26mm Expected efficiency: >65%

#### V. **TEST SETUP**

Input conditions: Vin: 80 – 275 VAC, 400 – 705 VDC Set Input current limit to 0.2A

Output: Variable resistive load to 200mA



### Equipment Used:

- 1. Isolated AC Source
- 2. High voltage DC source
- 3. Digital Oscilloscope
- 4. Multimeters
- 5. Electronic load

## Procedure:

- 1. Connect input terminals of the PMP7668 reference board to the AC/DC Power Source.
- 2. Connect output terminals to electronic load, maintaining correct polarity.
- 3. Maintain minimum load of about 2mA.
- 4. Gradually increase the input voltage from 0V to turn on voltage of 80VAC.
- 5. Observe the startup conditions for smooth switching waveforms.

#### VI. **BOARD ASSEMBLY DRAWINGS**





# VII. LAYOUT



# VIII. EFFICIENCY AND REGULATION

## a. Performance Data

AC Efficiency

	1		1	1	1	
Vin (VAC)	Pin (W)	VA	Vo (V)	lo (mA)	Po (W)	Efficiency (%)
80	1.29	2.77	9.51	100	0.95	73.5
100	2.01	4.29	9.52	150	1.43	71.0
110	2.84	6.04	9.53	200	1.91	67.2
130	2.77	6.03	9.53	200	1.91	68.7
150	2.73	6.24	9.53	200	1.91	69.9
170	2.70	6.51	9.53	200	1.91	70.5
190	2.69	6.80	9.53	200	1.91	70.9
210	2.68	7.09	9.53	200	1.91	71.0
230	2.68	7.37	9.53	200	1.91	71.0
250	2.68	7.64	9.53	200	1.91	71.0
275	2.69	7.95	9.53	200	1.91	70.8

DC Efficiency

Vin (VDC)	lin (mA)	Pin (W)	Vo (V)	lo (mA)	Po (W)	Efficiency (%)
400	6.49	2.60	9.53	200	1.91	73.42
500	5.28	2.64	9.53	200	1.91	72.20
600	4.50	2.70	9.53	200	1.91	70.59
705	3.93	2.77	9.53	200	1.91	68.79

February 27<sup>th</sup>, 2014



Regulation and Efficiency with output load

### b. Plots



🔱 Texas Instruments





February 27<sup>th</sup>, 2014

**TII - Reference Designs** 



# IX. WAVEFORMS

## a. Switching Node Waveforms



Vin = 110VAC, Full Load

Red trace: Drain voltage, 50V/div; Blue trace: Drain current, 500mA/div



<page-header><page-header>

19-Feb-14 11:15:48

Red trace: Drain voltage, 100V/div; Blue trace: Drain current, 500mA/div

# b. Output Ripple



9

# Vin = 110VAC, Full Load

LeCroy

19-Feb-14 11:16:13



## c. Turn On Characteristics



Vin = 110VAC, Full Load

Red trace: Input DC bus, 50V/div; Yellow trace: Output voltage, 5V/div



Red trace: Input DC bus, 100V/div; Yellow trace: Output voltage, 2V/div

# d. Transient response



# Vin = 230VAC, Load transient from 2mA to 200mA



# X. CONDUCTED EMISSIONS

230VAC Input, 200mA resistive load connected to PSU with short leads.

The conducted emissions in a pre-compliance test set-up were compared against EN55022 class B limits and found to be meeting them comfortably.







# XII. BILL OF MATERIALS

PMP7668 BOM Revision B							
Ite	Qt	Referenc				Manufactur	
m	y	е	Value	Description	Part Number	er	Size
							0.157 x
				Capacitor, Leaded, 760	PHE840MA6100KA04R		0.512
1	1 1 C1 0.1uf		0.1uF	VDC, ±10%	17	Kemet	inch
				Capacitor, Alum			10.00
2	2 2 C2, C3		10uF	Electrolytic 400V, ±20%	UCA2G100MPD1TD	Nichicon	mm Dia
				Capacitor, Alum Elect,			5 x 11
3	1	C4	10uF	25V, ±20%	Std	Std	mm
				Capacitor, Alum			8 x 11.5
4	1	C5	220 uF	Electrolytic, 25V, ±20%	25YXG220MEFC8X11.5	Rubycon	mm
				Capacitor, Ceramic Chip,			
5	2	C6, C7	0.1uF	X7R, 50V, ±10%	Std	Std	805
				Diode, Rectifier, 1000V,			
6	1	D1	1N4007	1A	1N4007	Diodes	DO-41
7	2	D2, D3	1N4937 Diode, Fast, 600V, 1A		1N4937	Fairchild	DO-41
							2.5 x
8	1	FR1	10	Fusible resistor, 0.5W	NFR25H0001009J	Vishay	7.5 mm
						Wurth	8.5 x
9	1	L1	4.7mH	Inductor, 150mA, 25ohm	744741472	Elektronik	5.5mm
						Wurth	7.8 x
10	1	L2	820uH	Inductor, 0.7A, 1.56ohm	7447728215	Elektronik	9.5mm
			KSC5026	Trans, NPN Medium	W6050361406	_ · · · · ·	70 406
11	1	Q1	M	Power, 800V, 1.5A	KSC5026MOS	Fairchild	10-126
12	1	R1	150K	Resistor, Chip, 1/4W, 1%	Std	Std	1206
13	1	R2	100K	Resistor, Chip, 1/8W, 1%	Std	Std	805
14	1	R3	0.75	Resistor, Chip, 1/2W, 5%	CRL1206-FW-R750ELF	Bourns	1206
		R4, R5,					
15	4	R6, R7	1M	Resistor, Chip, 1/4W, 5%	Std	Std	1206
16	1	R8	68.1K	Resistor, Chip, 1/8W, 1%	Std	Std	805
							10mm
17	1	RT1	510V	MOV, 510VAC	MOV-10D821KTR	Bourns	dia
	UCC2872 IC, CV/CC		IC, CV/CC PWM With				
18	1	U1	2	Primary Side Regulation	UCC28722DBV	ТІ	SOT-23
				IC, 24-V Input, 150 mA,			
				Utralow IQ LDO			
19	1	U2	TLV70433	Regulator	TLV70433DBV	TI	SOT-23



# XIII. CONCLUSION

The board is tested against the specifications given in section IV and found to meet them including an overall efficiency of >65% and a board form factor of <1800mm<sup>2</sup>. Also, the emission test performed in section X shows that this reference design is in compliance with EN55022 class B limits.



# XIV. APPENDIX

#### EVALUATION BOARD/KIT/MODULE (EVM) WARNINGS, RESTRICTIONS AND DISCLAIMER

For Feasibility Evaluation Only, in Laboratory/Development Environments. The EVM is not a complete product. It is intended solely for use for preliminary feasibility evaluation in laboratory / development environments by technically qualified electronics experts who are familiar with the dangers and application risks associated with handling electrical / mechanical components, systems and subsystems. It should not be used as all or part of a production unit.

#### Your Sole Responsibility and Risk. You acknowledge, represent and agree that:

- 1. You have unique knowledge concerning Federal, State and local regulatory requirements (including but not limited to Food and Drug Administration regulations, if applicable) which relate to your products and which relate to your use (and/or that of your employees, affiliates, contractors or designees) of the EVM for evaluation, testing and other purposes.
- 2. You have full and exclusive responsibility to assure the safety and compliance of your products with all such laws and other applicable regulatory requirements, and also to assure the safety of any activities to be conducted by you and/or your employees, affiliates, contractors or designees, using the EVM. Further, you are responsible to assure that any interfaces (electronic and/or mechanical) between the EVM and any human body are designed with suitable isolation and means to safely limit accessible leakage currents to minimize the risk of electrical shock hazard.
- Since the EVM is not a completed product, it may not meet all applicable regulatory and safety compliance 3. standards (such as UL, CSA, VDE, CE, RoHS and WEEE) which may normally be associated with similar items. You assume full responsibility to determine and/or assure compliance with any such standards and related certifications as may be applicable. You will employ reasonable safeguards to ensure that your use of the EVM will not result in any property damage, injury or death, even if the EVM should fail to perform as described or expected.

Certain Instructions. Exceeding the specified EVM ratings (including but not limited to input and output voltage, current, power, and environmental ranges) may cause property damage, personal injury or death. If there are questions concerning these ratings please contact a TI field representative prior to connecting interface electronics including input power and intended loads. Any loads applied outside of the specified output range may result in unintended and/or inaccurate operation and/or possible permanent damage to the EVM and/or interface electronics. Please consult the EVM User's Guide prior to connecting any load to the EVM output. If there is uncertainty as to the load specification, please contact a TI field representative. During normal operation, some circuit components may have case temperatures greater than 60°C as long as the input and output ranges are maintained at nominal These components include but are not limited to linear regulators, switching ambient operating temperature. transistors, pass transistors, and current sense resistors which can be indentified using the EVM schematic located in the EVM User's Guide. When placing measurement probes near these devices during normal operation, please be aware that these devices may be very warm to the touch.

Agreement to Defend, Indemnify and Hold Harmless. You agree to defend, indemnify and hold TI, its licensors and their representatives harmless from and against any and all claims, damages, losses, expenses, costs and liabilities (collectively, "Claims") arising out of or in connection with any use of the EVM that is not in accordance with the terms of this agreement. This obligation shall apply whether Claims arise under the law of tort or contract or any other legal theory, and even if the EVM fails to perform as described or expected.

Safety-Critical or Life-Critical Applications. If you intend to evaluate TI components for possible use in safetycritical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, such as devices which are classified as FDA Class III or similar classification, then you must specifically notify TI of such intent and enter into a separate Assurance and Indemnity Agreement.

#### **IMPORTANT NOTICE FOR TI REFERENCE DESIGNS**

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2014, Texas Instruments Incorporated