

How to Select Amplifiers for Pressure Transmitter Applications

Edward Mullins, Ian Williams, Giuseppe Lo Voi, Raphael Puzio



Introduction

Pressure transmitters are used to monitor weight, level, force and flow in industrial process control systems. The primary challenges encountered when designing pressure transmitters are nonlinearities and temperature dependence. Overcoming these challenges requires the proper implementation of an appropriate operational amplifier (OpAmp) and a deep understanding of, the precision, voltage range, and drive characteristics of the OpAmp.

Pressure Sensors

The four most common types of pressure sensors used in pressure transmitter applications are: Resistive, Capacitive, Silicon, and Linear Variable Differential Transformer (LVDT) with resistive strain gauges being the most commonplace. These four variants all use similar paths in the pressure transmitter signal chain. [Figure 1](#) illustrates a block diagram of a typical pressure transmitter signal path.

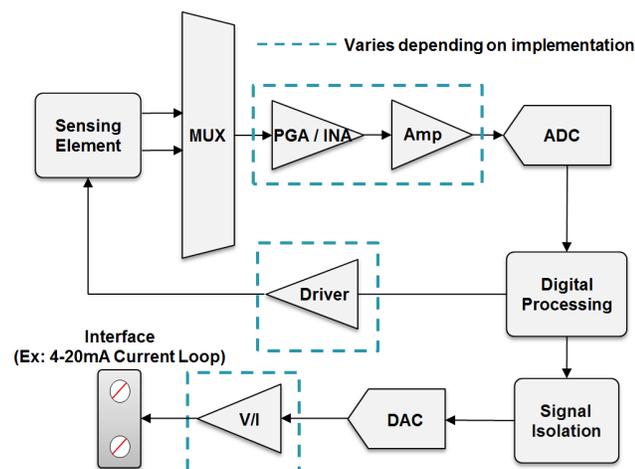


Figure 1. Common Pressure Transmitter Block Diagram

Various sensors and interfaces call for diverse device implementations.

- Instrumentation amplifiers, also known as INAs, are used to amplify small differential signals in the presence of larger or noisy common-mode signals
- Programmable-gain amplifiers, also known as

PGAs, can provide higher gain accuracy using selectable gain steps.

- Capacitive, LVDT and silicon sensors require implementation of a driver amplifier, which provides the excitation required for the sensor to capture changes in pressure or displacement.
- Voltage-to-current (V/I) converters are used to interface with commonly used 4-20mA current loops.

Instrumentation Amplifiers

The output signal from the sensing element will require amplification prior to digital conversion as sensor signals are typically very small and can commonly be in the low single millivolt range. Instrumentation amplifiers provide the necessary amplification while ensuring low noise and good rejection of the common-mode signals. The [INA828](#) is an INA, with super-beta input transistors that provide exceptionally low input offset, drift, noise, and optimized CMRR to help maintain signal accuracy when interfacing sensing elements.

Programmable Gain Amplifiers

Sensing elements typically output a nonlinear signal over temperature and pressure changes. A programmable gain amplifier with linearization circuitry, such as the [PGA309](#), can be used to adjust for nonlinearities. The [PGA309](#) is a programmable analog signal conditioner designed specifically for bridge sensors. The output of the [PGA309](#) is sufficient to drive any 5-V analog-to-digital converter (ADC). Any higher-voltage ADC must be buffered by a low-noise, low-offset voltage and low-drift OpAmp to extend the output signal and make use of the ADC's full dynamic range. The [OPA189](#) is a good option for a buffer amplifier, given its wide voltage range up to 36V, zero-drift and low-noise (5.8nV/ $\sqrt{\text{Hz}}$) performance.

Driver Amplifiers

Capacitive-, LVDT- and Silicon-based sensing elements require excitation by an OpAmp with sufficient drive characteristics necessary to enable the sensing element to capture minute changes in pressure and displacement. The important design

parameters for these OpAmps are output current and capacitive load drive. The [OPA196](#) OpAmp offers sufficient output current (65mA) and high capacitive load drive (1nF) capability making it a good choice for this application.

Table 1. Devices for Pressure Transmitter Applications

Device	Key Benefits
INA828	Very low-noise and high CMRR preserves optimum signal accuracy from low-level sensing elements.
INA333	Ultra-low power, high CMRR and zero-drift architecture minimize power consumption and eliminates common mode interference while enabling high accuracy over the full industrial temperature range.
PGA309	Maximize design versatility while mitigating pressure and temperature nonlinearities through highly integrated linearization circuit, fault monitoring and digital temperature compensation.
OPA189	Very low-noise, ultra-high CMRR and zero-drift architecture maximize signal accuracy and precision.
OPA196	High capacitive load drive (1 nF) and high output current (65mA) enables capacitive sensor excitation.
OPA187	Low-power and zero-drift architecture reduces power consumption and ensures high precision over the full industrial temperature range.
XTR115 XTR116	Integrated solutions for 4-to-20 mA loops provide low nonlinearity error and the convenience of an on-chip 5V voltage regulator and a precision VREF.
XTR300	Integrated 4-to-20mA loop solution: output can be configured as current or voltage without external shunt resistor and provides error flags and monitor pins for fault detection
XTR305	Cost effective version of XTR300. Integrated 4-to-20mA loop solution: output can be configured as current or voltage without external shunt resistor and provides error flags and monitor pins for fault detection.
XTR111	Simple 4-20mA driver provides an integrated device with low nonlinearity, good accuracy, wide supply and output error flag.

Voltage-to-Current Converters

A common interface in pressure transmitter applications is the 4-20mA current loop, which uses a precision, low-power OpAmp to create a measurable current range from a voltage range. The requisites of the OpAmp in this application are low power and high precision. The [OPA187](#), a new [zero-drift](#) OpAmp, features 10 μ V maximum offset and 100 μ A/channel quiescent current, making it a good candidate for such requirements. An integrated solution can also be implemented using an [XTR115](#), [XTR300](#), or [XTR305](#), which are precision current output converters designed to provide signal conditioning of low level signals and translation of them to a robust, noise-immune 4-20mA transmission.

Temperature, Power and Nonlinearities

In a real application environment, changes in temperature can affect the behavior of key device specifications, such as input offset voltage and input bias current. This impact can be mitigated by selecting [zero-drift](#) OpAmps. For applications with power constraints such as battery powered sensors or 4-20mA loops with many sensor nodes, low-power devices that maintain high precision are available. Nonlinearities in sensor output over pressure or temperature can be corrected by adjusting the excitation of the sensor. This function can be implemented through digital processing or integrated linearization circuitry.

Summary

The implementation of amplifiers in pressure transmitters will vary depending on sensing elements and interfaces. Issues with wide temperature drifts and nonlinearities can be mitigated through the proper use of Instrumentation amplifiers, programmable gain amplifiers and op amps. [Table 2](#) outlines some devices that are commonly used in pressure and field transmitter applications.

1 Related Documentation

Table 2. Related Articles and Resources

Media	Title
Technical Guide	TI Field Transmitter Solutions Guide
TI TechNotes	Offset Correction Methods
Application Report	Selecting an A/D Converter
TI Tech Note	Zero-drift Amplifiers: Features and Benefits

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated